

Chapter 35 Electric Circuits

Ohm's Law and Parallel Circuits

The equivalent resistance for resistors in parallel can be found using the following equation.

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$$

Calculate the current in a 48-V battery that powers three 15- Ω resistors connected in parallel.

1. Read and Understand

What information are you given?

voltage = $V = 48 \text{ V}$

individual resistances: $R_1 = R_2 = R_3 = 15 \text{ } \Omega$

2. Plan and Solve

What unknown are you trying to calculate?

current = $I = ?$

What equation can you use to find the unknown?

Ohm's law: $V = IR$

For a parallel circuit, $V = IR_{\text{eq}}$, where R_{eq} is the equivalent resistance.

Rearranging the equation gives you $I = \frac{V}{R_{\text{eq}}}$.

First, find the equivalent resistance R_{eq} .

$$\frac{1}{R_{\text{eq}}} = \frac{1}{15 \text{ } \Omega} + \frac{1}{15 \text{ } \Omega} + \frac{1}{15 \text{ } \Omega} = \frac{1}{5 \text{ } \Omega}$$

$$R_{\text{eq}} = 5 \text{ } \Omega$$

Then substitute for V and R_{eq} to solve for I .

$$I = \frac{48 \text{ V}}{5 \text{ } \Omega} = 9.6 \text{ A}$$

3. Look Back and Check

Is your answer reasonable?

Yes, a current of 9.6 A is reasonable, and the units are $\frac{\text{V}}{\Omega}$, or A, which is reasonable.

Math Practice

On a separate sheet of paper, solve the following problems.

1. Calculate the current in a 9-V battery that powers three 6- Ω resistors in parallel.

Chapter 35 Electric Circuits

2. Calculate the voltage impressed across a circuit in which three $1.5\text{-}\Omega$ resistors in parallel draw a current of 12 A .

3. Calculate the current in 12-V battery that powers four $10\text{-}\Omega$ resistors in parallel.