

WHAT HAPPENS TO THE READING ON THE GALVANOMETER WHEN THE SWITCH IN CIRCUIT 1 IS a) FIRST CLOSED, b) KEPT CLOSED, AND c) OPENED AGAIN?

